

ECE 41 FALL 05 COURSE PAGE

Classes T, R 4:00 - 5:15pm B-525, Recitations W 2:00 - 2:50pm B-426

Instructor: **Dr. Reed**, email: **Gregory.Reed@meppi.com**, office hours: T 5:15-6:00pm B-330

TA : **Narayan Krishnamurthy**, email: **nak54@pitt.edu**, office hours W 3:00 - 4:00pm B-1121C

There will be weekly recitations and homeworks for this course.

Homeworks will be assigned on Tuesday's and are due the following Thursday in Krishnamurthy's mailbox, in Room 340

Late submissions will incur 10% deduction.

NOTE: There is a change in the mailbox location, its in Sandy's room Benedum 340.

Home work

| | |
|---|---|
| HW1: 10.3.1,3.3,3.4, 10.4.1,4.3, 10.5.1,5.3,5.4,5.5,5.6 | due on 9/8 hw1 solution |
| HW2: 10.6.1,6.2, 10.7.2,7.4,7.6 10.8.1,8.2,8.3,8.4 | due on 9/15 hw2 solution |
| HW3: 10.9.1,9.2,9.3,9.4,9.5,9.6,9.8 10.10.1,10.2 | due on 9/22 hw3 solution |
| HW4: 10.10.3,10.4,10.8,10.9,10.11 10.11.1,11.3,11.4,11.5 | due on 9/29 hw4 solution |
| HW5: 10.12.1,12.3, 10.13.1,13.3 13.3.1,3.2,3.4,3.5,3.14 | due on 10/13 hw5 solution |
| HW6: 13.4.1,4.3,4.5,4.7,4.9 NOTE THERE IS A CORRECTION IN PBLM 13.4.5 | due on 10/20 hw6 solution |
| HW7: 11.3.1,3.2,3.3,3.4,3.5 11.4.1,4.3,4.5 | due on 10/27 hw7 solution |
| HW8: 11.5.1,5.2,5.3,5.5,5.7,5.8 11.6.2,6.4,6.5,6.9 | due on 11/3 hw8 solution |
| HW9: 12.3.1,3.2, 12.4.1,4.2,4.4,4.6, 12.5.1, 12.6.1,6.3 | due on 11/10 hw9 solution |
| HW10: 14.3.1,3.3,3.4 14.4.1,4.3,4.5 14.5.1,5.2,5.4,5.5 | due on 12/1 hw10 solution |
| HW11: 14.6.1,6.2,6.3 14.7.1,7.3,7.5 14.8.2 14.9.3 | due on 12/8 hw11 solution |
| HW12: 15.3.1,3.2,3.3 15.4.2,4.6 | hw12 solution |

Recitation

| | |
|--|-------------------------------|
| Exercise 10.3.2 Problems 10.3.2,3.6 | recitation 1 |
| Exercise 10.4.1,4.2, 10.5.1,5.2, 10.6.1,6.2,6.4 Problems 10.4.2, 10.5.7 | recitation 2 |
| Exercise 10.9.1, 9.2 Problems 10.8.5 10.9.7 | recitation 3 |
| Superposition, Thevenin Equivalent Ckt, Mesh Analysis; pblms 1 &3 on 9/21/05, to do pblms 2 and 4 on 9/28 | recitation 4 |
| Review Chapter 10 : Phasors, Mesh Analysis, Source Transformation, Impedences in series and parallel | recitation 5 |
| Network Function, Bode Plot | recitation 6 |
| Bode Plot Lecture notes 10/13 | lecture notes |
| Instantaneous Power, Effective Voltage, Average Power 10/26 | recitation 7 |
| Power factor, Complex Power 11/2 | recitation 8 |
| Laplace Transform, PFE Inv LT-repeated real roots, Time differentiation, time/frequency shifting, Initial & Final value theorem examples 11/15 | lecture notes |
| Laplace Transform contd, PFE Inv LT-Complex roots, solving differential equations - response of circuits | recitation 9 |
| HAVE A GOOD FINALS WEEK, IT WAS NICE BEING YOUR TA, THIS SEMS | THANK YOU |

Bode Plot

My Lecture ①
Notes 10/13/05.
To Dr Reed.
~ Narayanan

- Quick and dirty frequency response.

- Why do we use log scale?

- Compresses, meaning fully depict very small
Say 0.0001 $\xrightarrow{\log_{10}}$ -4

and very large values
Say 10000 $\xrightarrow{\log_{10}}$ 4

What is $|H(\omega)| = 5$ correspond to in dB

$$\begin{aligned} 20 \log\left(\frac{10}{2}\right) &= 20 \log 10 + 20 \log \frac{1}{2} \\ &= 20 - 6 \\ &= 14 \text{ dB} \end{aligned}$$


| $ H(j\omega) $ | $20 \log H(j\omega) $ |
|----------------------|------------------------|
| 1 | 0 |
| 2 | 6 dB |
| 3 | 9.54 dB |
| 10 | 20 dB |
| $\frac{1}{2}$ | -6 dB |
| $\frac{1}{\sqrt{2}}$ | -3 dB |
| $\sqrt{2}$ | 3 dB |
| 0.1 | -20 dB |

Determining Asymptotes of poles and zeros

① Single Zero @ $s = a$

$$H(s) = 1 + \frac{s}{a} = 1 + \frac{j\omega}{a}$$

$$|H(s)| = \sqrt{1 + \frac{\omega^2}{a^2}}$$

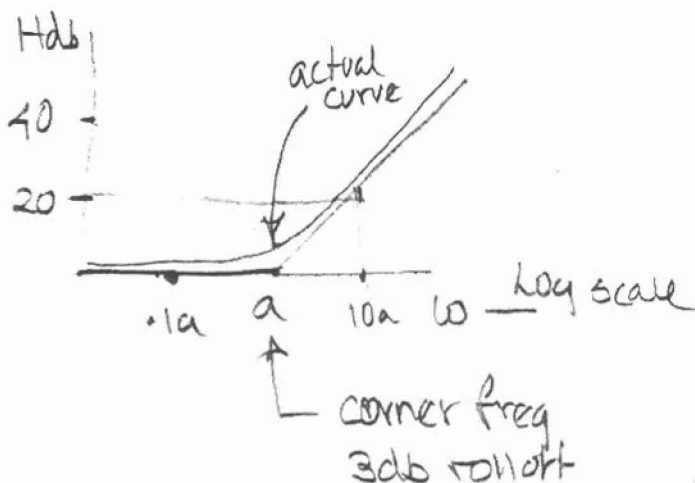


② Single pole @ $s=a$

②

$$H(s) = \frac{1}{1 + \frac{s}{a}} = \frac{1}{1 + \frac{j\omega}{a}}$$

$$|H(s)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{a}\right)^2}}$$

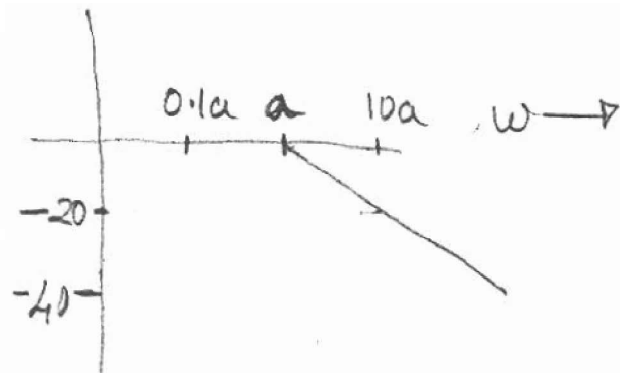

Eq

DC offset in freq response


Consider

$$H(s) = 20 \left(1 + \frac{s}{100} \right)$$

DC offset


$$20 \log H(0) = 20 \log 20 = 26 \text{ dB}$$

or
(0.1)
as the
case may
be

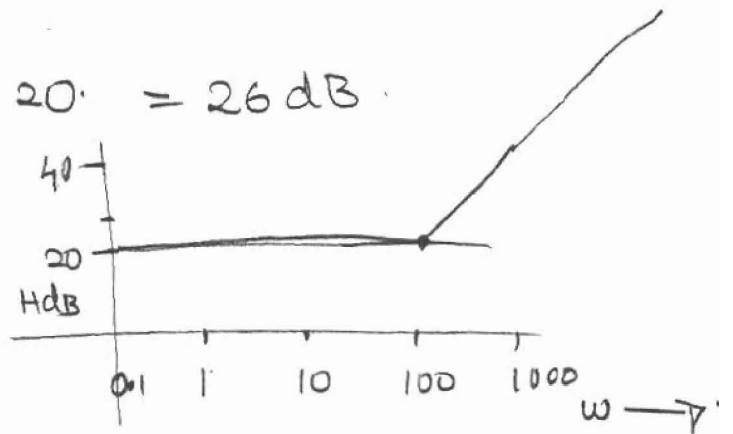


How would the
asymptotes look for

$$H(s) = s$$

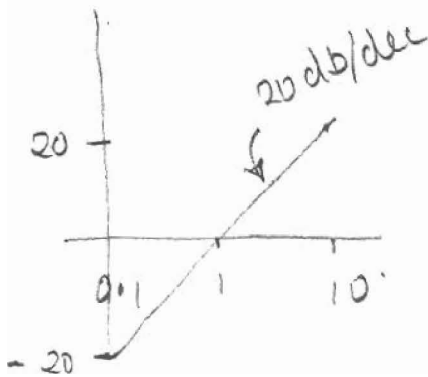

$$H(s) = \frac{1}{s}$$

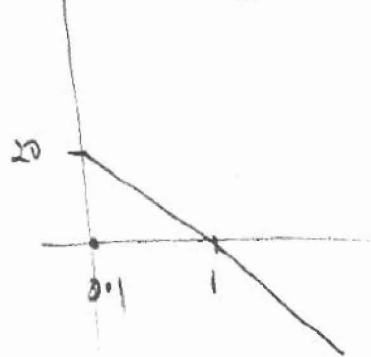

When poles and zeros are complex conjugate pairs:

$$H(s) = 1 + 2\xi \left(\frac{s}{\omega_0} \right) + \left(\frac{s}{\omega_0} \right)^2 \quad 0 < \xi < 1$$

$$\xi = 1 = 1 - \left(\frac{\omega}{\omega_0} \right)^2 + 2j\xi \left(\frac{\omega}{\omega_0} \right)$$

at $\omega = \omega_0$

$$H_{db} = 20 \log |0 + 2j|$$


= 6db roll off


$$\textcircled{a} \quad \omega = 0.5\omega_0$$

$$\xi = 0.25$$

$$H_{db} = 20 \log |1 - 0.25 + j2 \times 0.25 \times 0.5|$$

$$= -2.0db$$

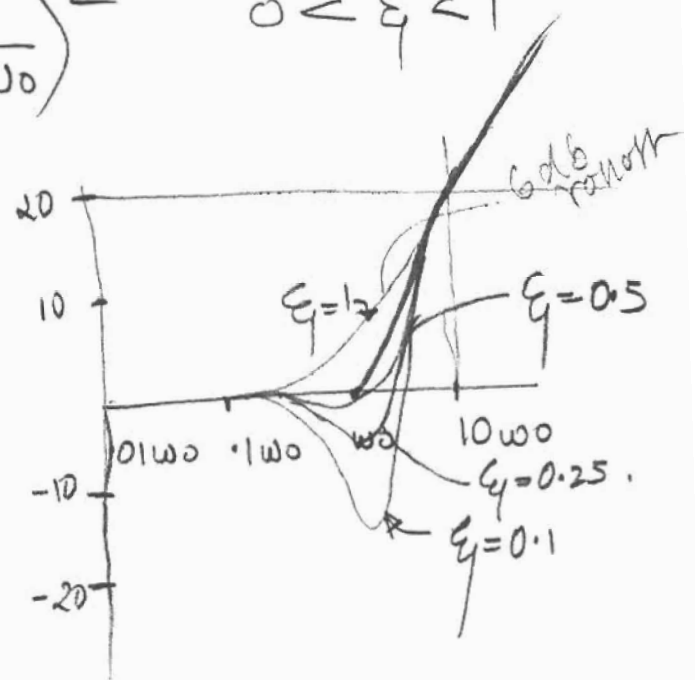

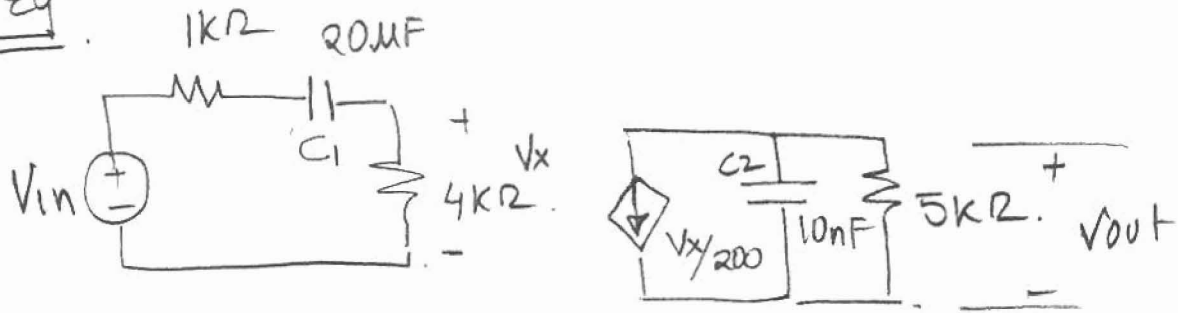Eg.

$H(\omega)$ can be found using Voltage division

$$V_x = \frac{V_{in} \cdot 4000}{5000 + \frac{1}{j\omega C_1}} \Rightarrow V_x(s) = \frac{V_{in}(s) \cdot 4000 \times 20e^{-6}}{1 + \frac{s}{10}}$$

$$V_{out} = \frac{V_x}{200} \cdot \frac{5000 \times \frac{1}{j\omega C_2}}{5000 + \frac{1}{j\omega C_2}} \Rightarrow V_{out}(s) = \frac{V_x(s)}{200} \cdot \frac{5000}{1 + \frac{s}{20000}}$$

$$V_{out} = \frac{V_{in}(s) \cdot 4000 \times 20e^{-6} \times 5000}{\left(1 + \frac{s}{10}\right) \cdot 200 \left(1 + \frac{s}{20000}\right)}$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{\frac{400}{200} s}{\left(1 + \frac{s}{10}\right) \left(1 + \frac{s}{20000}\right)} = \frac{2s}{\left(1 + \frac{s}{10}\right) \left(1 + \frac{s}{20000}\right)}$$


④


$$H(j\omega) = \begin{cases} 2j\omega & 1 < \omega < 10 \\ \frac{2j\omega}{\frac{j\omega}{10}} = 20 & 10 < \omega < 20 \\ \frac{2j\omega}{\frac{j\omega}{10} \cdot \frac{j\omega}{20000}} & \omega > 20000 \end{cases}$$


$$20 \log 20 = 26 \text{ db.}$$

↓

$$20 \log (10 \times 2) \nearrow$$

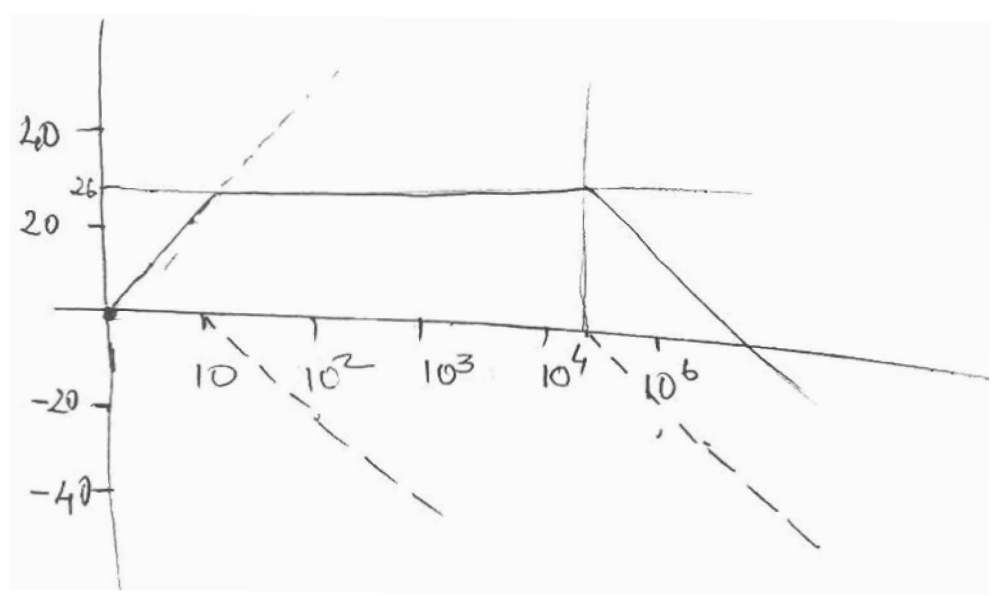

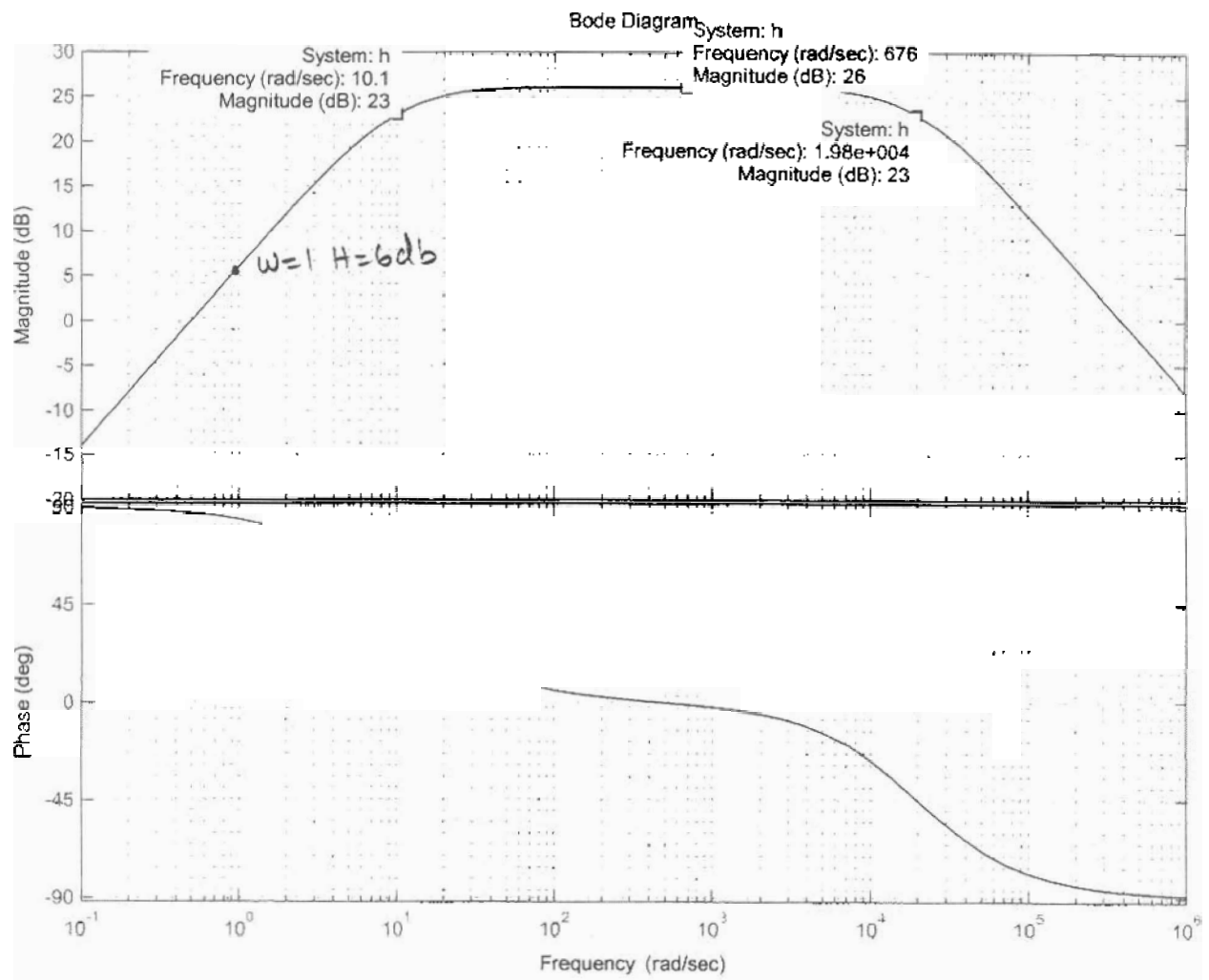

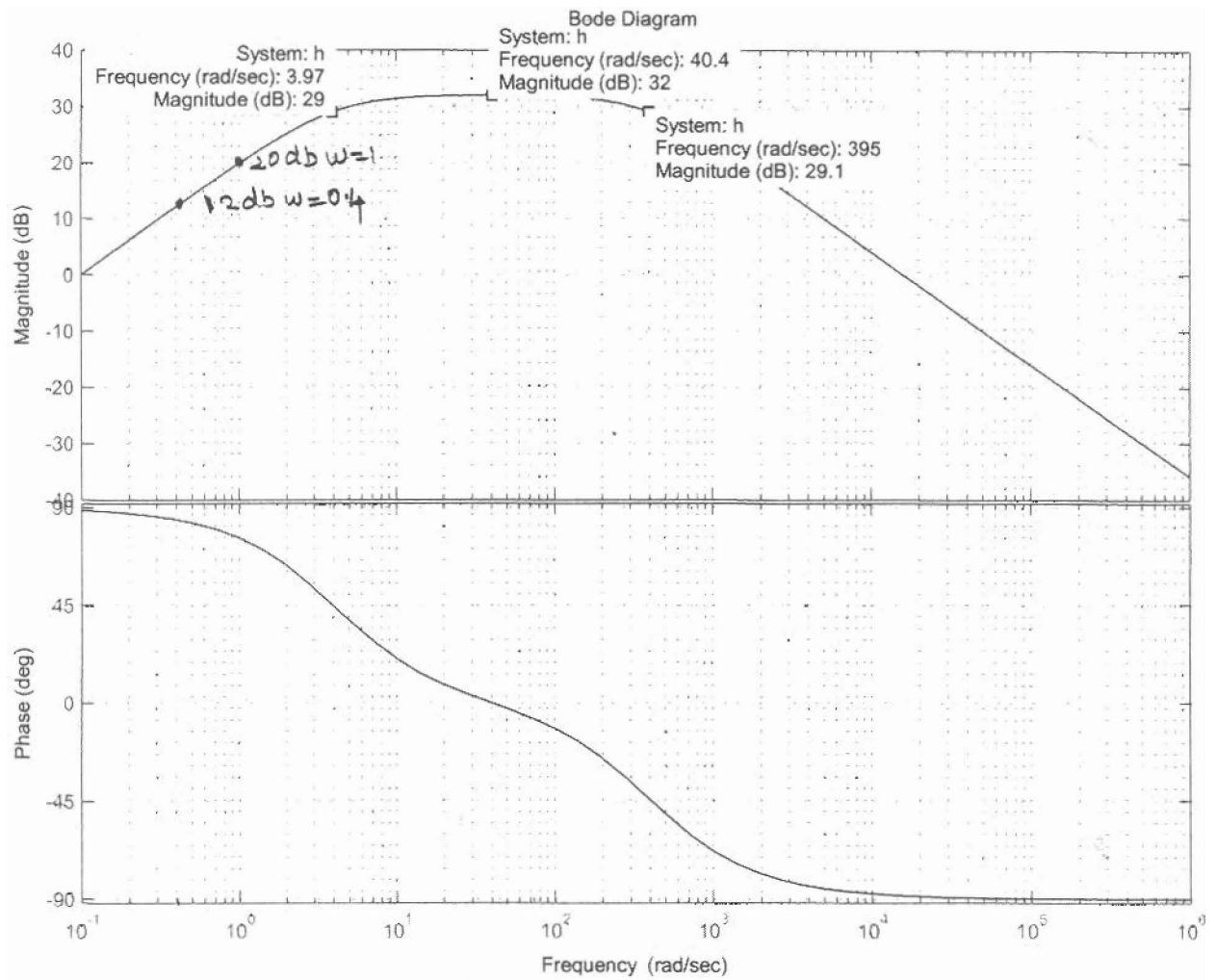


```
wmin = 0.1  
wmax = 10e5  
w = logspace(log10(wmin),log10(wmax))  
k = 0.05  
z = 1  
p1 = 40  
p2 = 400  
for i= 1:length(w)  
    h(i) = k*j*w(i)/((1 + j*w(i)/p1) * (1 + j*w(i)/p2));  
end  
subplot(211)  
semilogx(w, 20*log10(abs(h)))  
subplot(212)  
semilogx(w, angle(h).*180/pi)
```

```
wmin = 0.1  
wmax = 10e5  
w = logspace(log10(wmin),log10(wmax))  
  
%corrected 13.4.5  
h = tf([10 0],[6.25e-4 .2525 1.0000]);  
figure(1)  
bode(h,w)  
grid on
```

```
%pblm 16.9 pp581  
h = tf([2 0],[5e-6 .10005 1])  
figure(2)  
bode(h,w)  
grid on
```

Onesided Laplace transform — useful for analysis of ckts in TX domain, especially when forcing function is applied at say $t = t_0$. ①

$$F(s) = \int_{-\infty}^{\infty} f(t) u(t) e^{-st} dt = \int_{0^-}^{\infty} e^{-st} f(t) dt$$

Find LT of

$$f(t) = 2u(t-3)$$

$$F(s) = \int_{-\infty}^{\infty} f(t) e^{-st} dt = \int_3^{\infty} 2e^{-st} dt = \left. \frac{-2}{s} e^{-st} \right|_3^{\infty} = \frac{2e^{-3s}}{s}$$

Find LT of

$$f(t) = t e^{-t} u(t)$$

$$F(s) = \int_{-0}^{\infty} t e^{-t} \cdot e^{-st} dt$$

$$= \frac{-t \cdot e^{-(s+1)t}}{s+1} + \int \frac{e^{-(s+1)t}}{s+1}$$

$$= \frac{-t \cdot e^{-(s+1)t}}{s+1} - \frac{1 \cdot e^{-(s+1)t}}{(s+1)^2} \Big|_{-0}^{\infty}$$

$$= \frac{1}{(s+1)^2}$$

||| by

$$f(t) = t^n e^{-t} u(t) \quad F(s) = \frac{n!}{(s+1)^{n+1}}$$

$$\mathcal{L}(u(t)) = \int_0^{\infty} e^{-st} dt = \left. -\frac{1}{s} e^{-st} \right|_0^{\infty} = \frac{1}{s}$$

$$\mathcal{L}(s(t-t_0)) = \int_0^{\infty} e^{-st} s(t-t_0) dt = e^{-st_0}$$

$$\mathcal{L}(e^{-\kappa t} u(t)) = \int_0^{\infty} e^{-st} e^{-\kappa t} dt = \left. \frac{-1}{s+\kappa} e^{-(s+\kappa)t} \right|_0^{\infty} = \frac{1}{s+\kappa}$$

Inverse transforms for Rational functions.

$$H(s) = \frac{N(s)}{D(s)} \quad \begin{array}{l} \text{--- zeros} \\ \text{--- poles} \end{array} \quad \text{Use Partial fraction expansion}$$

$$H(s) = \frac{2}{s^3 + 12s^2 + 36s} = \frac{2}{s(s+6)^2}$$

$$\frac{a_1}{s} + \frac{a_2}{s+6} + \frac{a_3}{(s+6)^2} = \frac{2}{s(s+6)^2}$$

$$a_1(s+6)^2 + a_2(s+6)s + a_3s = 2$$

$$a_1(s^2 + 12s + 36) + a_2(s^2 + 6s) + a_3s = 2$$

Substituting a_1

$$\begin{array}{l} s^2 \\ s \\ \text{const} \end{array} \begin{bmatrix} 1 & 1 & 0 \\ 12 & 6 & 1 \\ 36 & 0 & 0 \end{bmatrix} \begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 2 \end{bmatrix}$$

$$\begin{bmatrix} a_1 \\ a_2 \\ a_3 \end{bmatrix} = S^{-1} \begin{bmatrix} 0 \\ 0 \\ 2 \end{bmatrix} = \begin{bmatrix} 1/18 \\ -1/18 \\ -1/3 \end{bmatrix}$$

$$V(s) = \frac{-1/3}{(s+6)^2} + \frac{-1/18}{s+6} + \frac{1/18}{s}$$

$$v(t) = \left[-\frac{1}{3} t e^{-6t} - \frac{1}{18} e^{-6t} + \frac{1}{18} \right] u(t)$$

time differentiation:

③

What is


$$\begin{aligned}\mathcal{L}\left\{\frac{df}{dt}\right\} &= \int_{0^-}^{\infty} e^{-st} \frac{df}{dt} dt \stackrel{\text{Integration by parts}}{=} \underbrace{e^{-st} f(t)}_{\text{boundary term}} - \int_{0^-}^{\infty} -s e^{-st} f(t) dt \\ &= e^{-st} f(t) \Big|_{0^-}^{\infty} + s F(s) = s F(s) - f(0^-)\end{aligned}$$

Similarly

$$\mathcal{L}\left\{\frac{d^2 f}{dt^2}\right\} = s^2 F(s) - s f(0^-) - f'(0^-)$$

$$\mathcal{L}\left\{\frac{d^3 f}{dt^3}\right\} = s^3 F(s) - s^2 f(0^-) - s f'(0^-) - f''(0^-)$$

Example

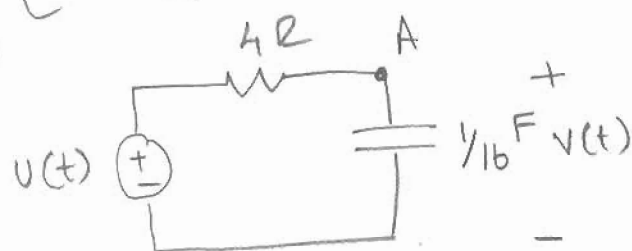

KCL @ A

$$\frac{V(t) - V(t)}{4} + \frac{1}{16} \frac{\partial V}{\partial t} = 0$$

$$V(0^-) = 9V$$

Taking LT:

$$\frac{V(s)}{4} - \frac{V(s)}{4} + \frac{1}{16} s V(s) - \frac{1}{16} V(0^-) = 0$$

$$V(s) \left[1 + \frac{s}{4} \right] = \frac{9}{4} + \frac{1}{s} = \frac{9s+4}{4s}$$

$$V(s) = \frac{9s+4}{4s} \times \frac{4}{(4+s)} = \frac{A}{s} + \frac{B}{s+4}$$

$$\boxed{V(t) = (1 + 8e^{-4t}) V(t)} \quad \text{PFE}$$

$$A = 1$$

$$B = \frac{-36+4}{-4} = 8$$

$$\mathcal{L}\{\sin \omega t u(t)\} = \frac{\omega}{s^2 + \omega^2} \quad \mathcal{L}\{\cos \omega t u(t)\} = \frac{s}{s^2 + \omega^2} \quad (4)$$

Initial Value & Final Value theorem.

$$\lim_{t \rightarrow 0^+} f(t) = \lim_{s \rightarrow \infty} s F(s)$$

$$\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} s F(s)$$

Example

$$f(t) = \cos(\omega_0 t) u(t)$$

$$f(0^+) = 1 \text{ clearly by substitution.}$$

From IVT

$$\lim_{s \rightarrow \infty} s \cdot \frac{s^2}{s^2 + \omega_0^2} \quad s \gg \omega_0^2$$

$$\rightarrow 1$$

Confirmed $f(0^+) = \lim_{s \rightarrow \infty} s F(s)$

$$f(t) = (1 - e^{-at}) u(t)$$

$$f(\infty) = 1 \text{ clear from substitution.}$$

From FVT

$$\lim_{s \rightarrow 0} s \cdot \left[\frac{1}{s} - \frac{1}{s+a} \right]$$

$$\lim_{s \rightarrow 0} \frac{a}{s+a} = \frac{a}{a} = 1$$

Confirmed

$$f(\infty) = \lim_{s \rightarrow 0} s F(s)$$

(5)

Use of time shifting Property

find LT of $f(t) = 3u(t-3)$

$$\mathcal{L}\{u\} = \frac{1}{s}$$

$$F(s) = \frac{3}{s} e^{-3s}$$

Direct Method

$$\text{LT of } 8e^{2t} [u(t+3) - u(t-3)]$$

Alternative Method:

$$\frac{8}{s-2} \left[e^{3(s-2)} - e^{-3(s-2)} \right]$$



$$\begin{aligned} \int_{-3}^3 8e^{2t} e^{-st} dt &= 8 \int_{-3}^3 e^{-(s-2)t} dt \\ &= -\frac{8}{s-2} e^{-(s-2)t} \Big|_{-3}^3 \\ &= \frac{-8}{s-2} \left[e^{-3(s-2)} - e^{+3(s-2)} \right] \end{aligned}$$

Find V_1 & V_2 By Superposition Theorem. RECITATION-4

9/21/05.


ANS:- $V_1 = 1 - j2$

$V_2 = -2 + j4$

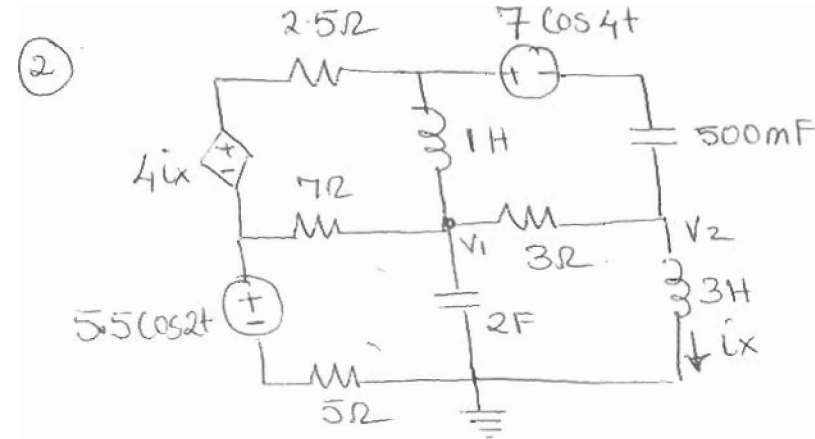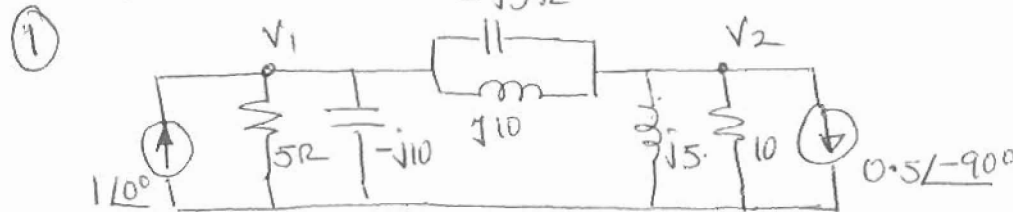

Note: Superposition of sources
i - Short ckt V sources
ii - Open ckt i sources.

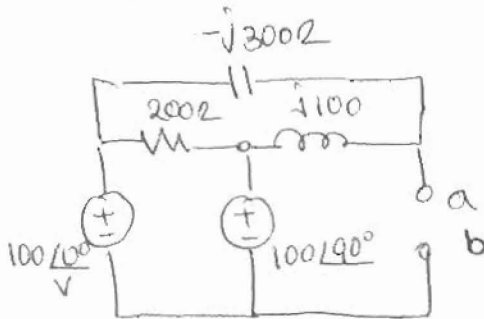
③ Find the thevenin Equivalent of the ckt.



ANS

$Z_{TH} = -j150\Omega$

$V_{TH} = 158.11 \angle 108.43^\circ$

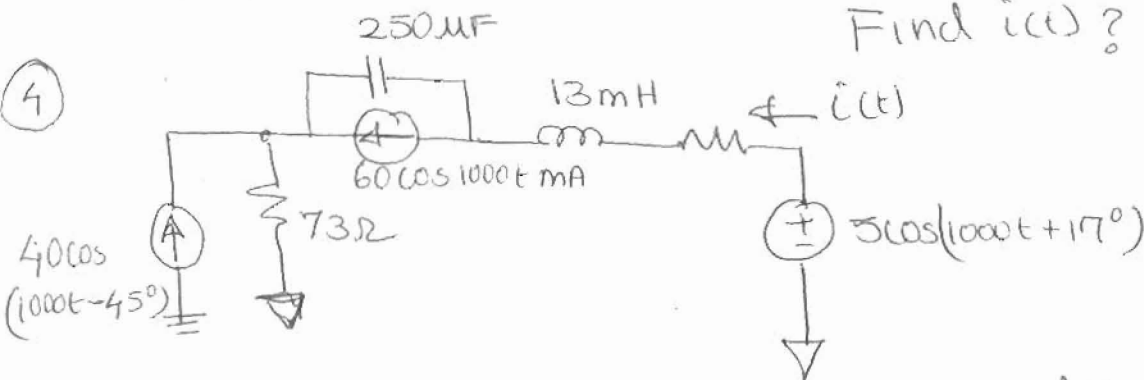

Find $i(t)$?

ANS:

$i(t) = 82.62 \angle -13.21^\circ \text{ mA}$

Chapter 10 - Review - RECITATION 5 - 9/28

① $V_1 = A_1 \cos(5t + 10^\circ)$ $V_2 = A_2 \sin(5t - 30^\circ)$
What is the relationship bet V_1 & V_2 - ?

② Equivalent Impedance - Series / parallel

Ans: V_1 leads V_2 by 130°

V_1 lags V_2 by 230°

Note 1: Phasors

$$I(t) = I_m \cos(\omega t + \phi)$$


$$I(t) = \text{Re} \{ I_m e^{j(\omega t + \phi)} \}$$

$$I = I_m e^{j\phi} = I_m \angle \phi$$

Note 2: KCL & KVL

Become vector addition of phasors

a) When a-b open, ab sckt

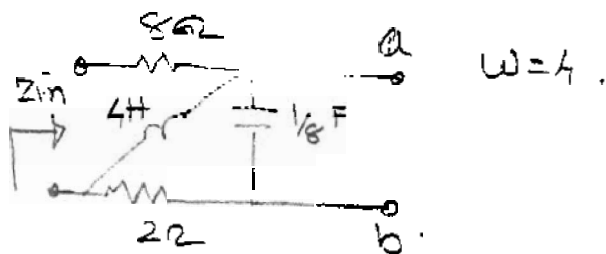


$$\omega = 4$$

Ans: ab open ab sckt

$$Z_{in} = 10.56 - 1.92j$$

$$Z_{in} = 9.97 + 0.246j$$

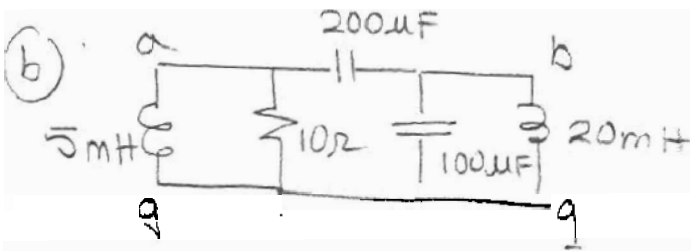


$$\omega = 1000 \text{ rad/s}$$

Find Z_{ag} , Z_{bg} , Z_{ab}

Ans $Z_{ag} = 2.8 + j4.5 \Omega$ $Z_{bg} = 1.8 - j1.2 \Omega$ $Z_{ab} = 0.11 - j3.8 \Omega$

③ Phasors & Mesh analysis

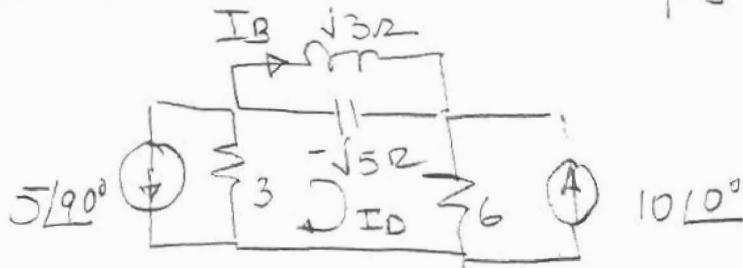

Find I_B & I_D ?

Ans:-

$$I_B = 13.19 \angle 154.23^\circ$$

$$I_D = 5.28 \angle 154.23^\circ$$

Recitation 6

What is


① 200mW is _____ in dBmW

Ans 23 dBmW.

50W in _____ dBW

Ans 17 dBW.

② Pblm. 13.3.9

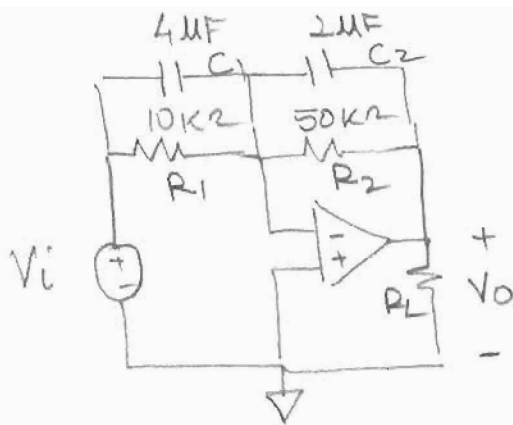Find gain $|H(\omega)|$

Phase shift at freq = 200 Hz


Ans: gain = 2.003

 $\angle H\omega = 140.7^\circ$

③ Ex 13.4-4

PP-586

④ Ex 13.4-6

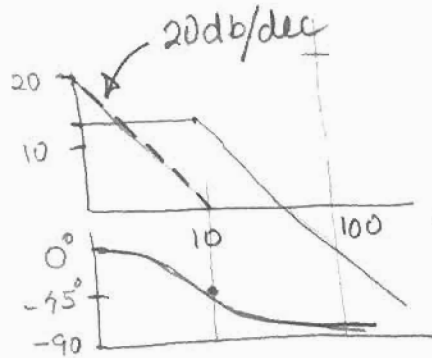


$$H(\omega) = 4.867 - 1.0026e^{2j}$$

$$\omega = 0.01 \text{ rad/s}$$

$$\omega \rightarrow \text{Ans } H(\omega) = \left(1 + \frac{R_1}{R_2}\right) \frac{1}{1 + j\omega CR}$$

$$\text{gain} = 100 \Rightarrow 40 \text{ dB}$$

$$\angle H(\omega) = -87^\circ$$

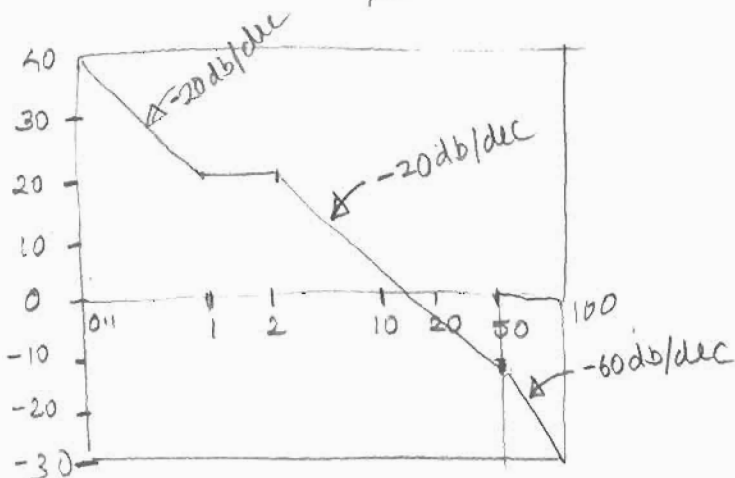

$$H(\omega) = \frac{10(1+s)}{s(1+0.5s)(12.5-j48.4+s)(12.5+j48.4+s)}$$

Recitation 7

① $i = 2t^2 - 1$ $1 < t < 3$


② 4H inductor what energy is delivered in $1 < t < 3$ ANS 576

③ 0.2F capacitor what power is delivered at $t = 2$ ANS
given $V(1) = 2$

Instantaneous power / energy.

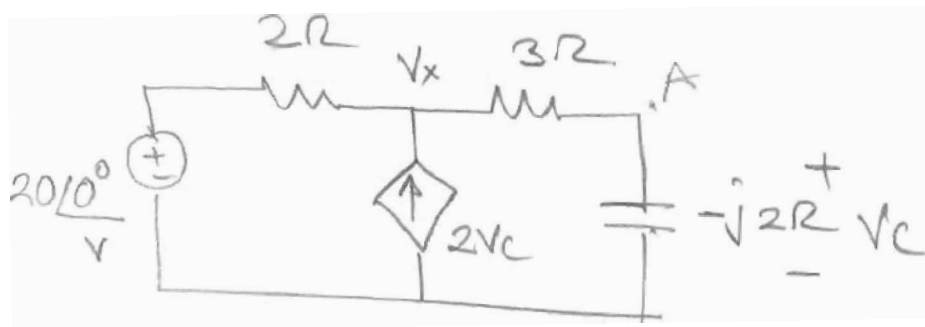142.331

④ What is the avg power supplied by the dependent source.




ANS = 26.23 W

⑤ ① Calculate effective value of
 $V(t) = 10 + 9 \cos 100t + 6 \sin 100t$

ANS: 12.59V

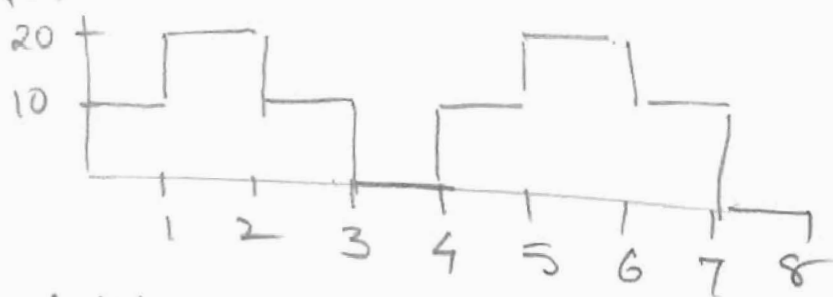② Find effective value of f where
 $f(t)$ is:




ANS: 12.247

③ Find avg of f

ANS: 10

④ If $V_C(0) = -2V$, $i_C(0) = 4A$ Find
Power absorbed by C @
a) $t = 0^+$ b) $0.2s$ c) $0.4s$.
ANS: -8W -0.554W 0.422W

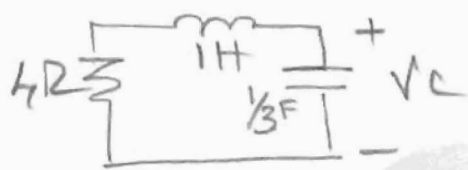

Recitation 8.

2/11/05.


- ① Find the effective value of waveform with $T=5s$

$$v(t) = 10 + [v(t) - v(t-2)] + 16e^{-0.5(t-3)} [v(t-3) - v(t-5)]$$


V_{eff}

$$= \sqrt{\frac{1}{5} \left[\int_0^2 100t^2 dt + \int_3^5 256e^{-0.5(t-3)} dt \right]}$$

$$= 9.879 \text{ . ANS}$$

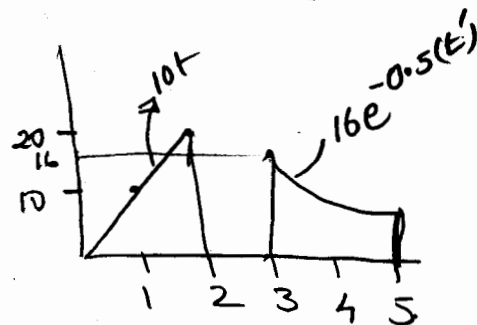

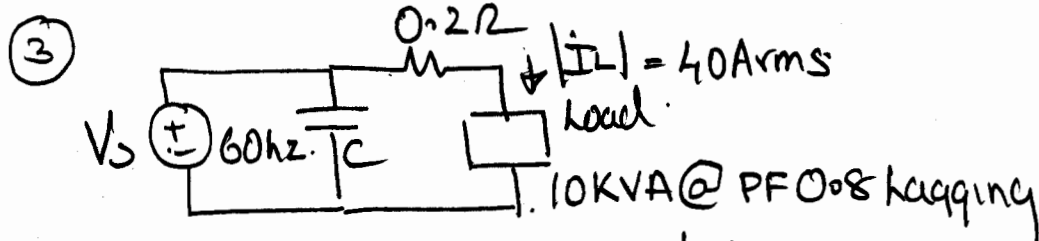- ② A series combination of inductor and Resistor must not dissipate more than 250mW, assuming sinusoidal i , $\omega=500 \text{ rad/s}$. What is the largest rms current in the ckt? $\text{ANS} = \underline{10.18 \text{ mA}_{rms}}$



What value of 'C' should cause the source to lag with PF 0.9. ?

$$\text{ANS: } C = \underline{79.5 \mu F}$$

- ④ A load operates at 2300 Vrms, draws 28 Arms, with PF=0.812 lagging. Find

a) Peak Current (39.6 A)

b) Instantaneous Power @ $t=2.5 \text{ ms}$, $f=60 \text{ Hz}$ (105.79 kW)

c) Real Power taken by load (52.29 kW)

d) Complex power (64.4 $\angle 35.7^\circ$ KVA)

e) Apparent Power (64.4 KVA)

f) Impedance of load (82.14 $\angle 35.7^\circ$)

g) Reactive Power (37.59 KVAR)

Recitation 9 - 11/30

① Find the $\mathcal{L}^{-1}[F(s)]$

Where

$$F(s) = 2 - \frac{1}{s} + \frac{25s^3 + 120s^2 + 220s + 240}{s^4 + 5s^3 + 8s^2 + 20s + 16}$$


Ans:-

$$f(t) = 2\delta(t) - u(t) + \frac{23}{3}e^{-t} + \frac{16}{3}e^{-4t} + 12\cos 2t + 12\sin 2t$$

② Pblm:-

14.7.2.

Find $i(t)$ for the ckt using LT

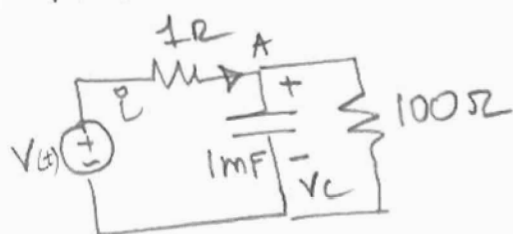

$$V(t) = 160 \cos 400t$$

$$V_c(0) = 0$$

$$\therefore i(0) = \frac{160 \cos(0)}{1} = 160 \text{ A}$$

Ans:-

$$i(t) = 136.9e^{-1010t} + 23 \cos 400t - 54.4 \sin 400t$$